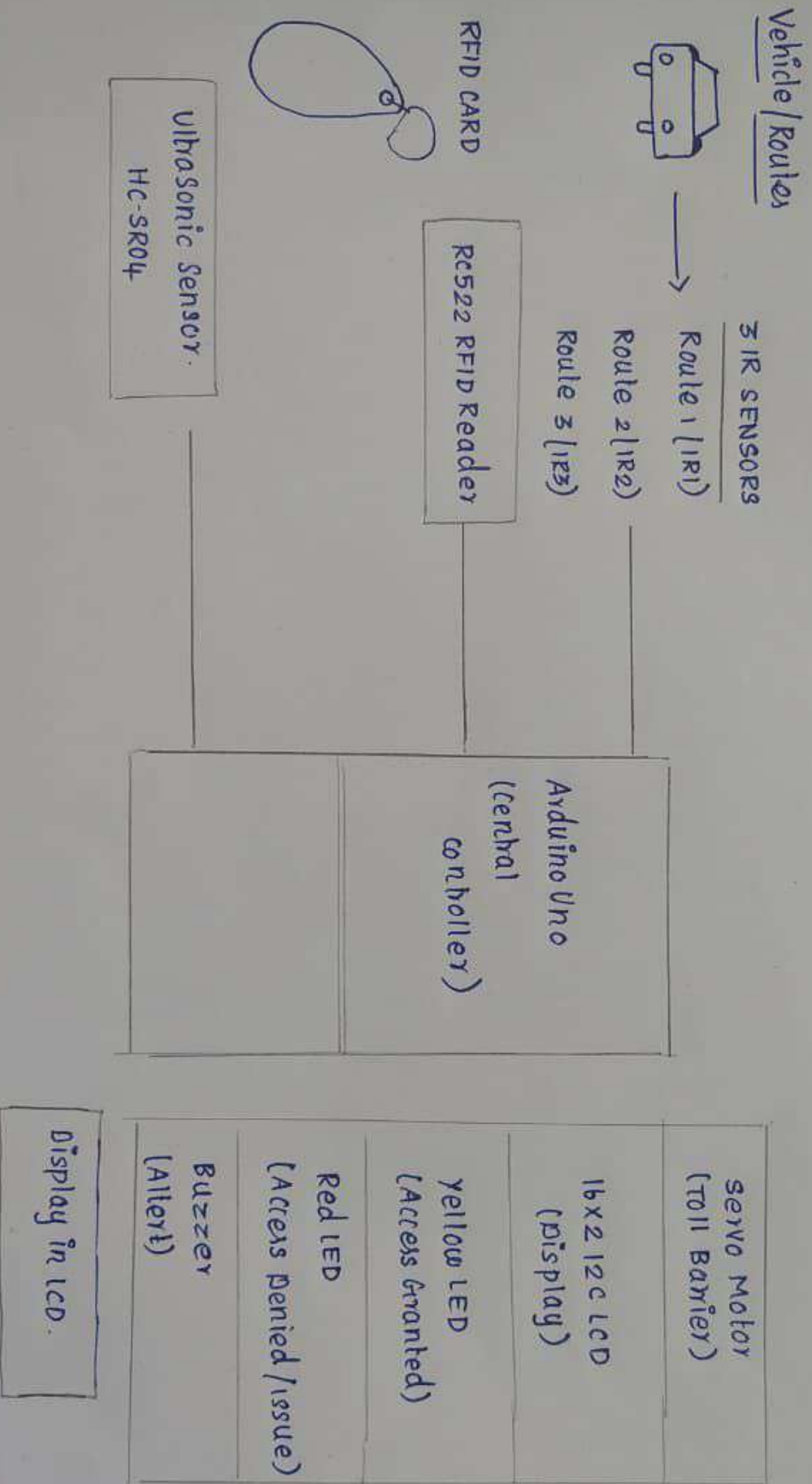




BLOCK DIAGRAM

SMART TOLL GATE & LCD MONITORING SYSTEM.




AGRI GUARD 360 – Schematic Diagram

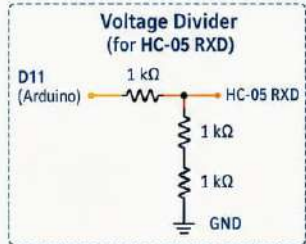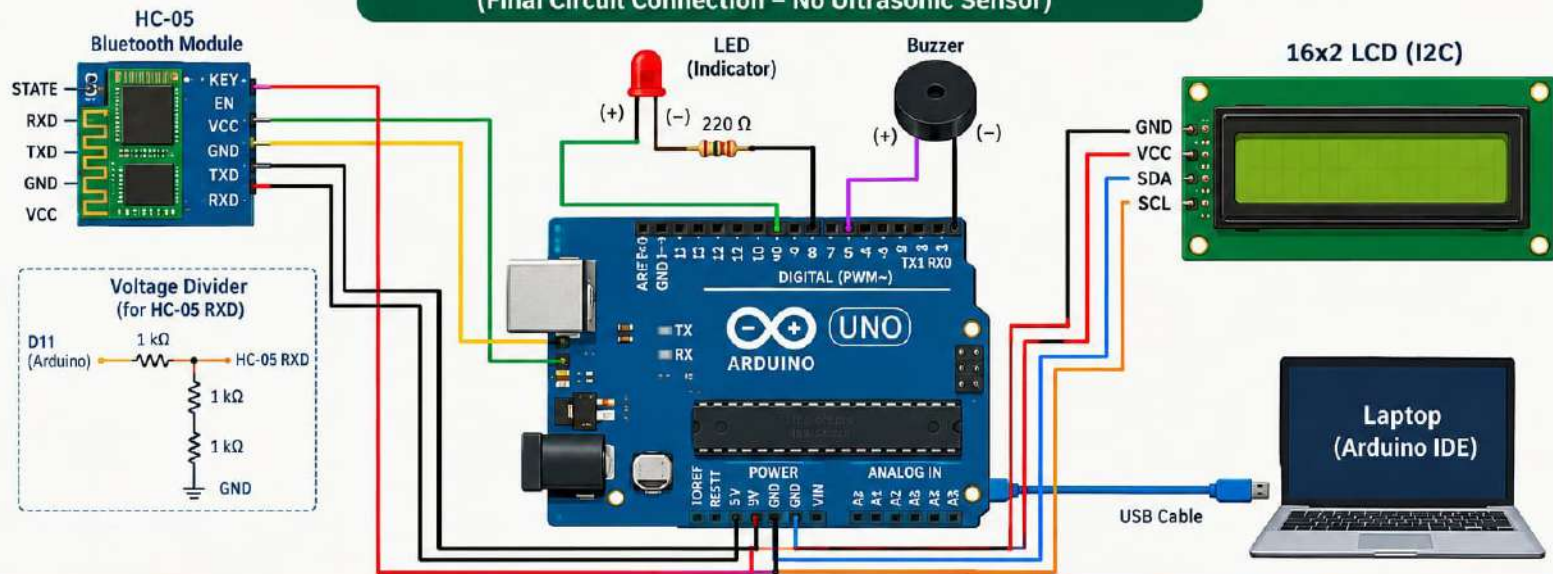(Final Circuit Connection – No Ultrasonic Sensor)



Component Connections		
Component	Pin	Arduino UNO
HC-05 Bluetooth	VCC	5V
	GND	GND
	TXD	D10
	RXD	D11 (through voltage divider)
16x2 LCD (I2C)	VCC	5V
	GND	GND
	SDA	A4
	SCL	A5

Other Connections		
Component	Pin	Arduino UNO
LED	Anode (+)	D13 (through 220Ω)
	Cathode (-)	GND
Buzzer	+	D8
	-	GND
Arduino → Laptop	USB port	USB cable
Arduino UNO = COM7 ✓		

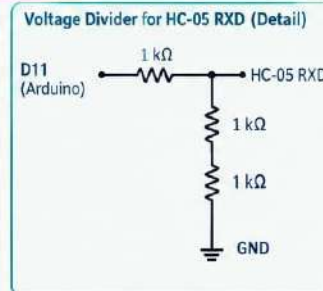

Wire Colour Guide	
Red	5V (VCC)
Black	GND
Yellow	D10 (HC-05 TXD)
Orange	D11 (HC-05 RXD)
Green	D13 (LED)
Purple	D8 (Buzzer)
Blue	A4 (LCD SDA)
Brown	A5 (LCD SCL)

AGRI GUARD 360 – Safe Fields • Smart Monitoring • Better Tomorrow